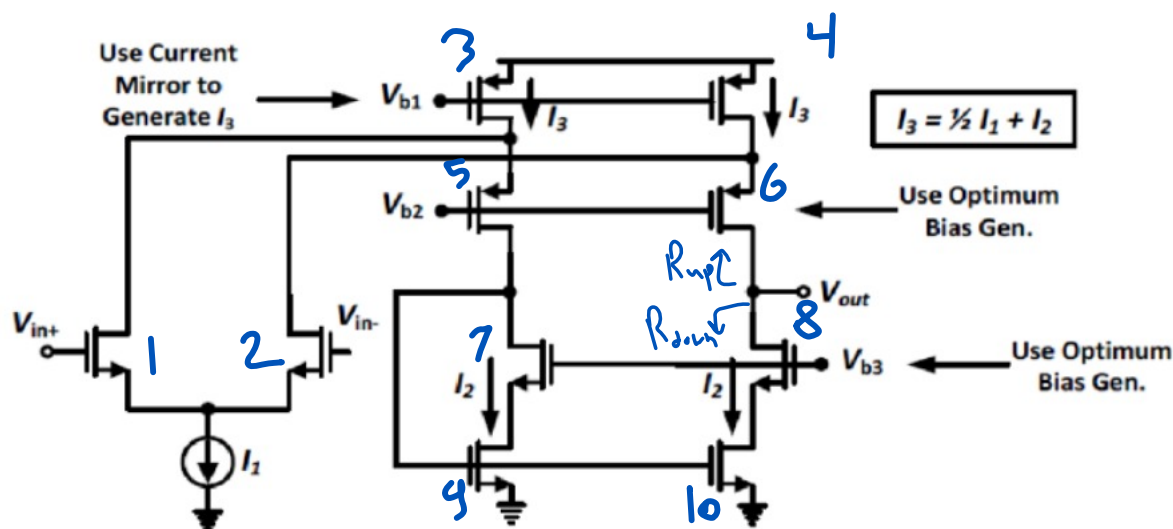


- Design steps
- Given specs
- Equations
- Assumptions
- Equivalent



1, 2 same  
:  
n, 2n same

- VDD = 3.3V
- VinCM = 0.5 \* VDD
- ADC (DC gain) > 58dB
- GBW > 150MHz for a load capacitance of 1pF
- Slew rate > 100 V/usec
- Output swing > 1.5 VPP
- Input referred noise density < 30nV /  $\sqrt{\text{Hz}}$  (include thermal and flicker only)
- PM > 60deg
- GM > 12dB
- Minimal power consumption and area.

①  $A = G_m R_{out}$

② (\*)  $G_m = g_{m2}$

③ (\*)  $R_{out} \approx (g_{m6} r_{o6} (r_{o4} \parallel r_{o2})) \parallel (g_{m8} r_{o8} r_{o10})$  }  $R_{out} = \frac{A}{g_{m2}} = \frac{58 \text{ dB}}{950 \mu} = 836.14 \text{ k}$   
let  $R_{out} = 836 \text{ k}$

④ (\*)  $GBW = \frac{G_m}{2\pi C_p} \rightarrow \frac{g_{m2}}{2\pi \times 1 \text{ pF}} > 150 \text{ M} \rightarrow g_{m2} > 942.5 \mu\text{S}$

let  $g_{m2} = 950 \mu\text{S}$

⑥ (\*)  $SR = \frac{I_{ss}}{C_p} \rightarrow \frac{I_1}{1 \text{ pF}} > 100 \text{ V}/\mu \rightarrow I_1 > 100 \mu\text{A}$

let  $I_1 = 110 \mu\text{A}$  also let  $I_2 = \frac{1}{2} I_1 = 55 \mu\text{A}$   
then  $I_3 = \frac{1}{2} I_1 + I_2 = 110 \mu\text{A}$

⑦  $V_{DSU}$  that makes 4 in sat

⑧ (\*)  $V_{out, max} = V_{DD} - (V_{DSat4} + V_{DSat6})$   
 $V_{out, min} = V_{DSat8} + V_{DSat10}$   
⑨ swing  $V_{out, max} - V_{out, min} > 1.5 \text{ VPP}$

assum all  $V_{DSat}$  are equal  
we get  $3.3 - 4 V_{DSat} > 1.5$

∴  $V_{DSat} < 0.45 \text{ V}$

while sizing  
if got one  
bigger must  
consumption with  
one smaller and etc...  
So overall is achieved

8

\* For any mos to be designed we need two values of  $\{g_m, r_o, I_D\}$

or one and ratio of two of them

lets start with input pair  $1, 2$

we have  $I_{D2} = \frac{1}{2} I_1 = 55 \mu A$  And  $g_{m2} = 950 \mu S$

Design  $\equiv$  get  $W$  &  $L$  of mos

But there is too much constraints that we need to consider

but as farmers in cadence we skip most of them

and follow known suggestion of experts in analog design

So for input pair we want relatively small  $L$  but  $\min \approx 400n \rightarrow \approx 600n$

let  $L_2 = 400n$  for low cap

in test bench we can't get real values for  $g_m$  but its ratio with  $I_D$  we can

So  $\frac{g_m}{I_D} \Big|_2 = 17.27 \rightarrow$  let  $\frac{g_{m2}}{I_{D2}} = 18$

now we plot  $\frac{g_m}{I_D}$  vs  $V_{GS}$  also  $I_D$  vs  $V_{GS}$

$I_D \propto W$  let basic  $W = 10\mu$  for reference

we get  $V_{GS} = 634 mV \rightarrow I_D = 13.42 \mu A$

but we need  $55 \mu$

So  $W_{new} = \frac{I}{(I_D/W)_{old}} = 41 \mu$

now edit  $W$  and rerun to get  $V_{DSat}$  and  $r_o$  as we need them in next steps

Got  $I_D = 54.45 \mu A$

$V_{DSat} = 78.57 mV$ ,  $r_o = 112.74 k$

+ 100 mV for stability

0.17857 V

9

3.4

\* Lets assume  $r_{o4} = r_{o2} = 112.7 k\Omega$  and we got  $I_3 = 110 \mu A$

but  $r_o$  changes greatly with  $I_D$  So we assume

$g_{m4} r_{o4} = 75$

which is weakly changes with  $I_D$

Run plot  $g_m r_o$  vs  $V_{GS}$  &  $I_D$  vs  $V_{GS}$  with

let  $L_4 = 400n$

and  $V_{DS4} = \frac{3}{4} V_{DD}$

@  $g_m r_o = 80 \rightarrow V_{GS} = 680.1 mV$ ,  $I_D = 17.83 \mu A$

$W_{new} = \frac{110}{\frac{17.83}{10}} = 61.7 \mu$

$I_{Dnew} = 109.6 \mu A$ ,  $V_{DSat} = 141.5 mV$ ,  $r_o = 51.38 k$

241.5 mV

Not what was intended but will be considered

10) AS for 5,6 we got  $R_{up} = g_{m6} r_{o6} (r_{o4} // r_{o2})$   
 $R_{down} = g_{m8} r_{o8} r_{o10}$

assume  $R_{up} = 2 R_{down}$

$$\therefore R_{out} = \frac{1}{3} R_{up} = 83,614 k \rightarrow R_{up} = 2,508 M\Omega$$

$$R_{down} = 1,254 M\Omega$$

we  $r_{o4} // r_{o2} = 35,29 k \rightarrow g_{m6} r_{o6} = 71 \rightarrow \text{perfect}$

assume  $g_{m6} r_{o6} = 75$

Run with  $V_{DS} = \frac{3,3}{4}$ ,  $I_{D1} = I_2 = 55 \mu A$

Let  $L_1 = 400 n$  same as the 3,4 but half current  $\rightarrow$  half width

$$W = 30,85 \mu$$

we Got

$$I_D = 55 \mu A, V_{GS} = 681,249 mV, V_{DSsat} = 141,679 mV, r_{o1} = 102,46 k$$

$$\rightarrow 241,679 mV$$

11)

7,8

$$R_{down} = g_{m8} r_{o8} r_{o10} = 1,254 M\Omega$$

assume  $g_{m8} r_{o8} = 85 \rightarrow r_{o10} = 14,75 k$

Run with  $V_{DS} = \frac{3,3}{4}$ ,  $I_D = I_2 = 55 \mu$

Let  $L = 700 n$  for low noise

$$\text{Got } V_{GS} = 931,28 mV, I_D = 150,79 \mu$$

$$\rightarrow W_{new} = 3,65 \mu$$

$$\text{Final} \rightarrow I_D = 54,75, V_{DSsat} = 282,45 mV, r_{o1} = 270,55 k$$

$$\rightarrow 382,45 mV$$

12)

9,10

$$r_{o10} = 14,75 k, I_D = 55 \mu, V_{DS} = \frac{3,3}{4}$$

let  $g_{m10} r_{o10} = 75$  use

$$L = 400 n$$

$$\text{we get } V_{GS} = 740,118 mV, I_D = 58,856 \mu A$$

$$\rightarrow W_{new} = 9,34 \mu$$

$$\text{Final} \rightarrow I_D = 54,9 \mu, V_{DSsat} = 136,48 mV, r_{o1} = 123,77 k$$

$$\rightarrow 236,48 mV$$

final  $R_{out}$

$$= 2,646 M // 10,5 M$$

$$= 2,1 M \text{ good for now}$$

13

(\*) Current mirror pair of  $I_1$

$$V_{DS} = 1,45V,$$